

Multiple Choice

19.1 Ohm's law 30.

What are the SI units for electric current?

- a. C/s
- b. e/s
- c. $-\text{e}/\text{s}$
- d. C/s^2

31.

What quantity is used to describe the ability of a material to limit current flow?

- a. C/m
- b. C/s
- c. Ω
- d. V

32.

The equivalent unit for an ohm is a _____.

- a. V/A
- b. C/m
- c. $\frac{\text{A}}{\text{V}}$
- d. V/s

33.

You put 9.0 V DC across resistor R_1 and measure the current through it. With the same voltage across resistor R_2 , you measure twice the current. What is the ratio $\frac{R_1}{R_2}$?

- a. 1
- b. $\frac{1}{2}$
- c. 4
- d. 2

19.2 Series Circuits 34.

What does the circuit element shown represent?



- a. a battery
- b. a capacitor
- c. the ground
- d. a switch


35.

How many $10\text{-}\Omega$ resistors must be connected in series to make an equivalent resistance of $80\text{ }\Omega$?

- a. 80
- b. 8
- c. 20
- d. 40

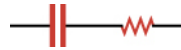36.

Which two circuit elements are represented in the circuit diagram?



- a. a battery connected in series with an inductor
- b. a capacitor connected in series with a resistor
- c. a resistor connected in series with a battery
- d. an inductor connected in series with a resistor

37.

How much current will flow through a 10-V battery with a $100\text{-}\Omega$ resistor connected across its terminals?

- a. 0.1 A
- b. 1.0 A
- c. 0
- d. $1,000\text{ A}$


19.3 Parallel Circuits 38.

A $10\text{-}\Omega$ resistor is connected in parallel to another resistor R . The equivalent resistance of the pair is $8\text{ }\Omega$. What is the resistance R ?

- a. $10\text{ }\Omega$
- b. $20\text{ }\Omega$
- c. $30\text{ }\Omega$
- d. $40\text{ }\Omega$

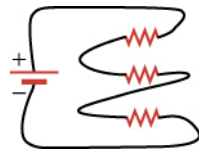39.

Are the resistors shown connected in parallel or in series? Explain.



- a. The resistors are connected in parallel because the same current flows through all three resistors.

- b. The resistors are connected in parallel because different current flows through all three resistors.
- c. The resistors are connected in series because the same current flows through all three resistors.
- d. The resistors are connected in series because different current flows through all three resistors.

19.4 Electric Power 40.

Which equation below for electric power is incorrect?

- a. $P = I^2 R$
- b. $P = \frac{V}{R^2}$
- c. $P = IV$
- d. $P = \frac{V^2}{R}$

41.

What power is dissipated in a circuit through which 0.12 A flows across a potential drop of 3.0 V ?

- a. 0.36 W
- b. 0.011 W
- c. Voltage drop across is 5 V .
- d. 2.5 W

42.

How does a resistor dissipate power?

- a. A resistor dissipates power in the form of heat.
- b. A resistor dissipates power in the form of sound.
- c. A resistor dissipates power in the form of light.
- d. A resistor dissipates power in the form of charge.

43.

What power is dissipated in a circuit through which 0.12 A flows across a potential drop of 3.0 V ?

- a. 0.36 W
- b. 0.011 W
- c. 5 V
- d. 2.5 W