

Extended Response

19.1 Ohm's law 61.

Explain how current and charge are related, including how direction is defined.

- Current is the ratio of charge passing through a conductor per unit time. The current's direction is the direction in which protons would flow.
- Charge is the ratio of current passing through a conductor per unit time. The charge's direction is the direction in which protons would flow.
- Current is the product of charge passing through a conductor and the amount of time that passes. The current's direction is the direction in which electrons would flow.
- Charge is the product of current passing through a conductor and time. The charge's direction is the direction in which electrons would flow.

62.

Under what conditions might a resistor material that normally follows Ohm's law become non-ohmic?

- If the amount of current flowing through the material is too low, the resistor may heat up, creating a nonlinear relationship between current and voltage.
- If the amount of current flowing through the material is too high, the resistor may heat up, creating a nonlinear relationship between current and voltage.
- If the amount of current flowing through the material is too low, the resistor may not warm up enough to allow a nonlinear relationship between current and voltage.
- If the amount of current flowing through the material is too high, the resistor may not warm up enough to allow a nonlinear relationship between current and voltage.


63.

You connect a single resistor R across a 10 V battery and find that 0.01 A flows through the circuit. You add another resistor R after the first resistor and find that 0.005 A flows through the circuit. If you have 10 resistors R connected in a line one after the other, what would be their total resistance?

- $\frac{R}{10}$
- $5R$
- $\frac{10}{R}$
- $10R$

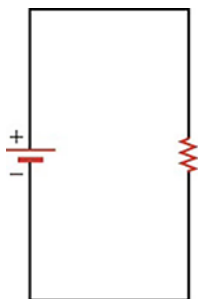19.2 Series Circuits 64.


Explain why the current is the same at all points in the circuit below.



- a. If the current were not constant, the mobile charges would bunch up in places, which means that the voltage would decrease at that point. A lower voltage at some point would push the current in the direction that further decreases the voltage.
- b. If the current were not constant, the mobile charges would bunch up in places, which means that the voltage would increase at that point. But a higher voltage at some point would push the current in the direction that decreases the voltage.
- c. If the current were not constant, the mobile charges would bunch up in places, which mean that the voltage would increase at that point. A higher voltage at some point would push the current in the direction that further increases the voltage.
- d. If the current were not constant, the mobile charges would bunch up in places, which mean that the voltage would decrease at that point. But a lower voltage at some point would push the current in the direction that increases the voltage.

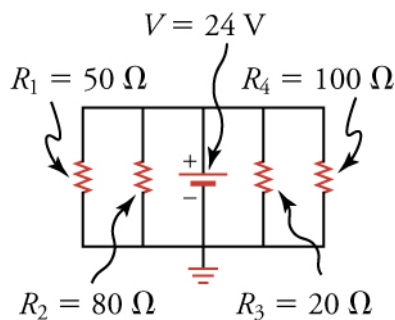65.

What is the current through each resistor in the circuit?



- a. Current through resistors R_1 , R_2 , R_3 , and R_4 is 0.48 A, 0.30 A, 1.2 A, and 0.24 A, respectively.
- b. Current through resistors R_1 , R_2 , R_3 , and R_4 is 1200 A, 1920 A, 480 A, and 2400 A, respectively.
- c. Current through resistors R_1 , R_2 , R_3 , and is R_4 2.08 A, 3.34 A, 0.833 A,

and 4.17 A, respectively.

- d. The same amount of current, 0.096 A, flows through all of the resistors.

19.3 Parallel Circuits 66.

Power is supplied to a circuit in a house by one incoming wire at high potential compared with the ground. How does the voltage at each outlet on the circuit change and why?

- a. All outlets on the circuit have the same voltage because they are wired in parallel.
- b. All outlets on the circuit have the same voltage because they are wired in series.
- c. Outlets further away from the source have a lower voltage because they are wired in parallel.
- d. Outlets further away from the source have a lower voltage because they are wired in series.

19.4 Electric Power 67.

A single resistor is connected across the terminals of a battery. When you attach a second resistor in parallel with the first, does the power dissipated by the system change?

- a. No, the power dissipated remain same.
- b. Yes, the power dissipated increases.
- c. Yes, the power dissipated decreases.

68.

In a flashlight, the batteries are normally connected in series. Why are they not connected in parallel?

- a. Batteries are connected in series for higher voltage and power output.
- b. Batteries are connected in series for lower voltage and power output.
- c. Batteries are connected in series so that power output is a much lower for the same amount of voltage.
- d. Batteries are connected in series to reduce the overall loss of energy from the circuit.