

## Key Terms

**alternating current** electric current whose direction alternates back and forth at regular intervals

**ampere** unit for electric current; one ampere is one coulomb per second (  $1 \text{ A} = 1 \text{ C/s}$  )

**circuit diagram** schematic drawing of an electrical circuit including all circuit elements, such as resistors, capacitors, batteries, and so on

**conventional current** flows in the direction that a positive charge would flow if it could move

**direct current** electric current that flows in a single direction

**electric circuit** physical network of paths through which electric current can flow

**electric current** electric charge that is moving

**electric power** rate at which electric energy is transferred in a circuit

**equivalent resistor** resistance of a single resistor that is the same as the combined resistance of a group of resistors

**in parallel** when a group of resistors are connected side by side, with the top ends of the resistors connected together by a wire and the bottom ends connected together by a different wire

**in series** when elements in a circuit are connected one after the other in the same branch of the circuit

**nonohmic** material that does not follow Ohm's law

**Ohm's law** electric current is proportional to the voltage applied across a circuit or other path

**ohmic** material that obeys Ohm's law

**resistance** how much a circuit element opposes the passage of electric current; it appears as the constant of proportionality in Ohm's law

**resistor** circuit element that provides a known resistance

**steady state** when the characteristics of a system do not change over time