

PHYS11 CH:19 The Invisible River of Energy

How Charge Flows Through the World

Mr. Gullo

December 2025

Outline

- 1 Introduction
- 2 19.1 Ohm's Law
- 3 19.2 Series Circuits
- 4 19.3 Parallel Circuits
- 5 19.4 Electric Power
- 6 Summary

What if you could control
an invisible river of charge?

What if you could control
an invisible river of charge?

From nerve impulses in your brain to hydroelectric dams sending power across continents...

What if you could control
an invisible river of charge?

From nerve impulses in your brain to hydroelectric dams sending power across continents...

Same laws guide the flow.

The Invisible River



The Invisible River



The Mental Model

Electric current is like water flowing through pipes - voltage is the pressure, resistance is the friction.

Learning Objectives

By the end of this section, you will be able to:

- **19.1:** Describe how current is related to charge and time

Learning Objectives

By the end of this section, you will be able to:

- **19.1:** Describe how current is related to charge and time
- **19.1:** Distinguish between direct and alternating current

Learning Objectives

By the end of this section, you will be able to:

- **19.1:** Describe how current is related to charge and time
- **19.1:** Distinguish between direct and alternating current
- **19.1:** Define resistance and verbally describe Ohm's law

Learning Objectives

By the end of this section, you will be able to:

- **19.1:** Describe how current is related to charge and time
- **19.1:** Distinguish between direct and alternating current
- **19.1:** Define resistance and verbally describe Ohm's law
- **19.1:** Calculate current and solve problems involving Ohm's law

19.1 The Flow of Charge

The Definition

$$I = \frac{\Delta Q}{\Delta t}$$

Current equals charge per unit time. Measured in amperes (A).

19.1 The Flow of Charge

The Definition

$$I = \frac{\Delta Q}{\Delta t}$$

Current equals charge per unit time. Measured in amperes (A).

One ampere = one coulomb per second: $1 \text{ A} = 1 \text{ C/s}$

19.1 The Flow of Charge

The Definition

$$I = \frac{\Delta Q}{\Delta t}$$


Current equals charge per unit time. Measured in amperes (A).

One ampere = one coulomb per second: $1 \text{ A} = 1 \text{ C/s}$


The Mental Model

If 5 coulombs flow past a point in 1 second, the current is 5 A.

19.1 The Direction Paradox

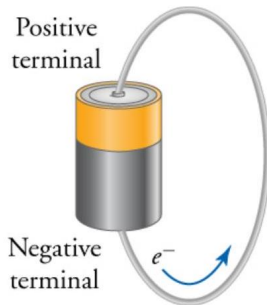

19.1 The Direction Paradox

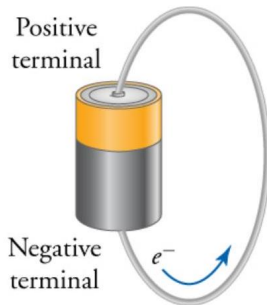

The Paradox

Reality: Electrons flow from negative to positive.

Convention: Current flows from positive to negative.

19.1 Direct Current vs Alternating Current

Direct Current (DC)

- Flows one direction
- Constant over time
- Batteries provide DC

19.1 Direct Current vs Alternating Current

Direct Current (DC)

- Flows one direction
- Constant over time
- Batteries provide DC

Alternating Current (AC)

- Direction alternates
- Smoothly reverses
- Wall sockets provide AC


19.1 Direct Current vs Alternating Current

Direct Current (DC)

- Flows one direction
- Constant over time
- Batteries provide DC

Alternating Current (AC)

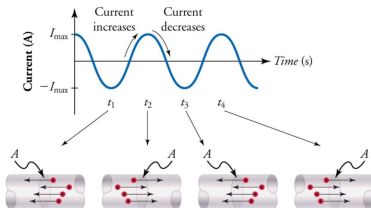- Direction alternates
- Smoothly reverses
- Wall sockets provide AC



19.1 The Universal Law of Resistance

Ohm's Law

$$V = IR$$

Voltage equals current times resistance. The pushback equation.

19.1 The Universal Law of Resistance

Ohm's Law

$$V = IR$$

Voltage equals current times resistance. The pushback equation.

Units: Resistance measured in ohms (Ω), where $1\Omega = 1 \text{ V/A}$

19.1 The Universal Law of Resistance

Ohm's Law

$$V = IR$$

Voltage equals current times resistance. The pushback equation.

Units: Resistance measured in ohms (Ω), where $1\Omega = 1 \text{ V/A}$

The Mental Model

Resistance is friction for electrons - it converts electrical energy to heat.

Attempt: Lightning Strike Current

The Challenge (3 min, silent)

A lightning strike transfers 10^{20} electrons from cloud to ground in 2 ms.

Given:

- $n = 10^{20}$ electrons
- $e = -1.60 \times 10^{-19} \text{ C}$
- $\Delta t = 2 \times 10^{-3} \text{ s}$

Find: Average current I

Can you calculate the current in a lightning bolt? Work silently.

Compare: Lightning Strike

Turn and talk (2 min):

- 1 How did you find the total charge?
- 2 What formula did you use for current?
- 3 What sign did you get for your answer?

Compare: Lightning Strike

Turn and talk (2 min):

- 1 How did you find the total charge?
- 2 What formula did you use for current?
- 3 What sign did you get for your answer?

Name wheel: One pair share your approach (not your answer).

Reveal: The Power of Lightning

Self-correct in a different color:

Step 1: Total charge: $\Delta Q = ne = (10^{20})(-1.60 \times 10^{-19} \text{ C}) = -16.0 \text{ C}$

Reveal: The Power of Lightning

Self-correct in a different color:

Step 1: Total charge: $\Delta Q = ne = (10^{20})(-1.60 \times 10^{-19} \text{ C}) = -16.0 \text{ C}$

Step 2: Current: $I = \frac{\Delta Q}{\Delta t}$

Reveal: The Power of Lightning

Self-correct in a different color:

Step 1: Total charge: $\Delta Q = ne = (10^{20})(-1.60 \times 10^{-19} \text{ C}) = -16.0 \text{ C}$

Step 2: Current: $I = \frac{\Delta Q}{\Delta t}$

$$I = \frac{-16.0 \text{ C}}{2 \times 10^{-3} \text{ s}} = \boxed{-8 \text{ kA}}$$

Reveal: The Power of Lightning

Self-correct in a different color:

Step 1: Total charge: $\Delta Q = ne = (10^{20})(-1.60 \times 10^{-19} \text{ C}) = -16.0 \text{ C}$

Step 2: Current: $I = \frac{\Delta Q}{\Delta t}$

$$I = \frac{-16.0 \text{ C}}{2 \times 10^{-3} \text{ s}} = \boxed{-8 \text{ kA}}$$

Check: Negative sign means electrons flow down. Conventional current flows up!

Attempt: Headlight Resistance

The Challenge (3 min, silent)

An automobile headlight has 2.50 A flowing through it when 12.0 V is applied.

Given:

- $I = 2.50 \text{ A}$
- $V = 12.0 \text{ V}$

Find: Resistance R of the headlight

Can you find the resistance using Ohm's law?

Compare: Resistance

Turn and talk (2 min):

- 1 What equation did you start with?
- 2 How did you solve for R ?
- 3 What units did you get?

Compare: Resistance

Turn and talk (2 min):

- 1 What equation did you start with?
- 2 How did you solve for R ?
- 3 What units did you get?

Name wheel: One pair share your approach.

Reveal: Headlight Resistance

Self-correct in a different color:

Start with Ohm's law: $V = IR$

Reveal: Headlight Resistance

Self-correct in a different color:

Start with Ohm's law: $V = IR$

Solve for R: $R = \frac{V}{I}$

Reveal: Headlight Resistance

Self-correct in a different color:

Start with Ohm's law: $V = IR$

Solve for R: $R = \frac{V}{I}$

Substitute: $R = \frac{12.0 \text{ V}}{2.50 \text{ A}}$

Reveal: Headlight Resistance

Self-correct in a different color:

Start with Ohm's law: $V = IR$

Solve for R: $R = \frac{V}{I}$

Substitute: $R = \frac{12.0 \text{ V}}{2.50 \text{ A}}$

$$R = 4.8\Omega$$

Reveal: Headlight Resistance

Self-correct in a different color:

Start with Ohm's law: $V = IR$

Solve for R: $R = \frac{V}{I}$

Substitute: $R = \frac{12.0 \text{ V}}{2.50 \text{ A}}$

$$R = 4.8\Omega$$

Check: 4.8 ohms - relatively small resistance for a headlight.

Learning Objectives

By the end of this section, you will be able to:


- **19.2:** Interpret circuit diagrams and diagram basic circuit elements

Learning Objectives


By the end of this section, you will be able to:

- **19.2:** Interpret circuit diagrams and diagram basic circuit elements
- **19.2:** Calculate equivalent resistance of resistors in series

19.2 The Language of Circuits

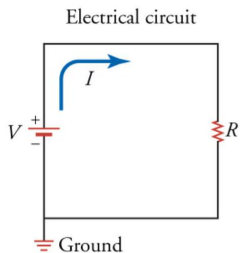


(a)

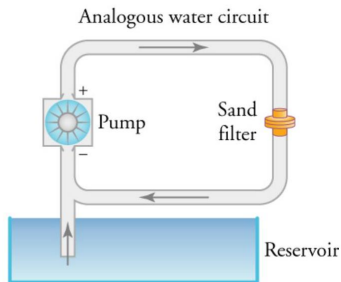


(b)

19.2 The Language of Circuits

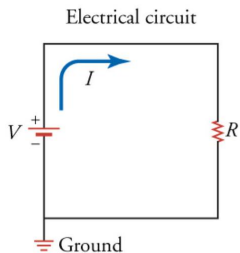

(a)

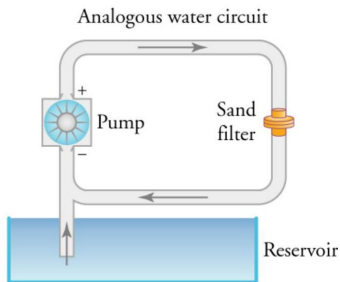


(b)


Circuit symbols:

- Battery: long line = positive, short line = negative
- Resistor: zigzag element
- Wire: perfect conductor (no resistance)
- Ground: reference point (voltage = 0)

19.2 Resistors in Series

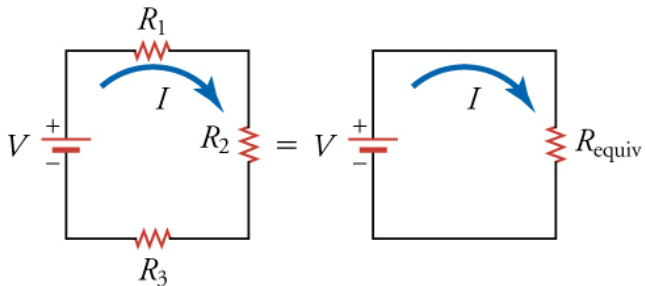

19.2 Resistors in Series

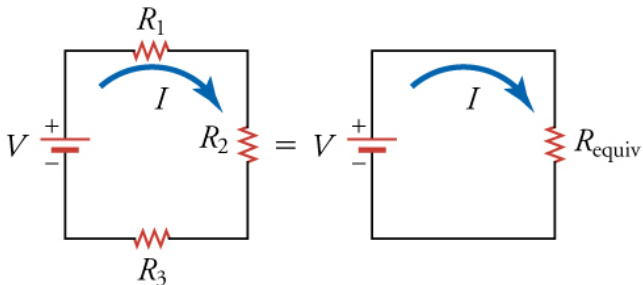

The Rule for Series

$$R_{\text{equiv}} = R_1 + R_2 + R_3$$

Series resistances add. One path, obstacles accumulate.

19.2 The Voltage Loop

Key insight: Going around a complete loop, voltage changes sum to zero.

19.2 The Voltage Loop

Key insight: Going around a complete loop, voltage changes sum to zero.

The Mental Model

Like hiking in hills - total elevation gained equals total elevation lost when you return to start.

19.2 The Voltage Loop

Key insight: Going around a complete loop, voltage changes sum to zero.

The Mental Model

Like hiking in hills - total elevation gained equals total elevation lost when you return to start.

For series circuit: $V_{\text{battery}} = V_1 + V_2 + V_3$

19.2 The Voltage Loop

Key insight: Going around a complete loop, voltage changes sum to zero.

The Mental Model

Like hiking in hills - total elevation gained equals total elevation lost when you return to start.

For series circuit: $V_{\text{battery}} = V_1 + V_2 + V_3$

Using Ohm's law: $V = I(R_1 + R_2 + R_3)$

Attempt: Series Circuit

The Challenge (3 min, silent)

Three resistors in series: $R_1 = 1.0\Omega$, $R_2 = 6.0\Omega$, $R_3 = 13\Omega$. Battery voltage is 12 V.

Given:

- $R_1 = 1.0\Omega$, $R_2 = 6.0\Omega$, $R_3 = 13\Omega$
- $V = 12\text{ V}$

Find: (a) Equivalent resistance, (b) Current through circuit

Can you reduce the circuit to a single resistance?

Compare: Series Resistance

Turn and talk (2 min):

- 1 How did you find equivalent resistance?
- 2 What equation did you use for current?
- 3 Did you get the same values?

Compare: Series Resistance

Turn and talk (2 min):

- 1 How did you find equivalent resistance?
- 2 What equation did you use for current?
- 3 Did you get the same values?

Name wheel: One pair share your approach.

Reveal: Series Solution

Self-correct in a different color:

Part (a): $R_{\text{equiv}} = R_1 + R_2 + R_3$

Reveal: Series Solution

Self-correct in a different color:

Part (a): $R_{\text{equiv}} = R_1 + R_2 + R_3$

$$R_{\text{equiv}} = 1.0\Omega + 6.0\Omega + 13\Omega = \boxed{20\Omega}$$

Reveal: Series Solution

Self-correct in a different color:

Part (a): $R_{\text{equiv}} = R_1 + R_2 + R_3$

$$R_{\text{equiv}} = 1.0\Omega + 6.0\Omega + 13\Omega = \boxed{20\Omega}$$

Part (b): $I = \frac{V}{R_{\text{equiv}}}$

Reveal: Series Solution

Self-correct in a different color:

Part (a): $R_{\text{equiv}} = R_1 + R_2 + R_3$

$$R_{\text{equiv}} = 1.0\Omega + 6.0\Omega + 13\Omega = \boxed{20\Omega}$$

Part (b): $I = \frac{V}{R_{\text{equiv}}}$

$$I = \frac{12\text{ V}}{20\Omega} = \boxed{0.60\text{ A}}$$

Reveal: Series Solution

Self-correct in a different color:

Part (a): $R_{\text{equiv}} = R_1 + R_2 + R_3$

$$R_{\text{equiv}} = 1.0\Omega + 6.0\Omega + 13\Omega = \boxed{20\Omega}$$

Part (b): $I = \frac{V}{R_{\text{equiv}}}$

$$I = \frac{12\text{ V}}{20\Omega} = \boxed{0.60\text{ A}}$$

Check: Voltage drops: $V_1 = 0.6\text{ V}$, $V_2 = 3.6\text{ V}$, $V_3 = 7.8\text{ V}$. Sum = 12 V!

Learning Objectives

By the end of this section, you will be able to:


- **19.3:** Interpret circuit diagrams with parallel resistors

Learning Objectives


By the end of this section, you will be able to:

- **19.3:** Interpret circuit diagrams with parallel resistors
- **19.3:** Calculate equivalent resistance of resistor combinations

19.3 Resistors in Parallel

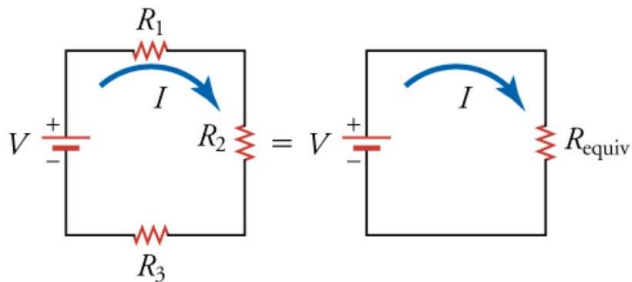

19.3 Resistors in Parallel

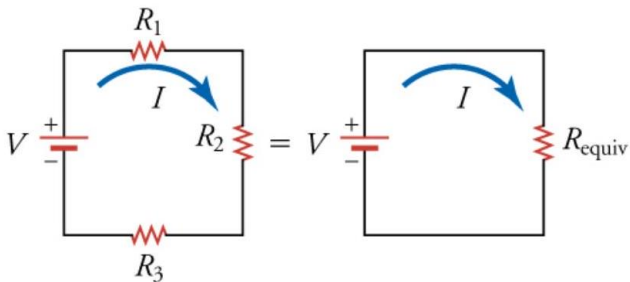

The Rule for Parallel

$$R_{\text{equiv}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

Parallel resistance is reciprocal of sum of reciprocals.

19.3 The Parallel Paradox

What Your Brain Gets Wrong

Intuition: More resistors means more resistance.

Reality: Parallel resistors provide MORE paths, so LESS resistance!

19.3 The Parallel Paradox

What Your Brain Gets Wrong

Intuition: More resistors means more resistance.

Reality: Parallel resistors provide MORE paths, so LESS resistance!

Key insight: R_{equiv} is always LESS than smallest resistor in parallel.

19.3 The Parallel Paradox

What Your Brain Gets Wrong

Intuition: More resistors means more resistance.

Reality: Parallel resistors provide MORE paths, so LESS resistance!

Key insight: R_{equiv} is always LESS than smallest resistor in parallel.

The Mental Model

Three identical resistors R in parallel: $R_{\text{equiv}} = R/3$

19.3 Current Conservation

Key principle: Current entering a junction equals current leaving.

19.3 Current Conservation

Key principle: Current entering a junction equals current leaving.

For parallel resistors: $I = I_1 + I_2 + I_3$

19.3 Current Conservation

Key principle: Current entering a junction equals current leaving.

For parallel resistors: $I = I_1 + I_2 + I_3$

The Mental Model

Like a river splitting into three channels - total water flow is conserved.

19.3 Current Conservation

Key principle: Current entering a junction equals current leaving.

For parallel resistors: $I = I_1 + I_2 + I_3$

The Mental Model

Like a river splitting into three channels - total water flow is conserved.

Using Ohm's law on each: $I = V\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)$

Attempt: Parallel Circuit

The Challenge (3 min, silent)

Three resistors in parallel: $R_1 = 10\Omega$, $R_2 = 25\Omega$, $R_3 = 15\Omega$. Battery voltage is 3 V.

Given:

- $R_1 = 10\Omega$, $R_2 = 25\Omega$, $R_3 = 15\Omega$
- $V = 3\text{ V}$

Find: (a) Equivalent resistance, (b) Total current

Can you use the reciprocal formula?

Compare: Parallel Resistance

Turn and talk (2 min):

- 1 How did you handle the reciprocals?
- 2 What calculator steps did you use?
- 3 Is your answer less than 10 ohms?

Compare: Parallel Resistance

Turn and talk (2 min):

- 1 How did you handle the reciprocals?
- 2 What calculator steps did you use?
- 3 Is your answer less than 10 ohms?

Name wheel: One pair share your approach.

Reveal: Parallel Solution

Self-correct in a different color:

Part (a): $R_{\text{equiv}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$

Reveal: Parallel Solution

Self-correct in a different color:

Part (a): $R_{\text{equiv}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$

$$R_{\text{equiv}} = \frac{1}{\frac{1}{10} + \frac{1}{25} + \frac{1}{15}} = \frac{1}{0.1 + 0.04 + 0.0667} = \boxed{4.84\Omega}$$

Reveal: Parallel Solution

Self-correct in a different color:

Part (a): $R_{\text{equiv}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$

$$R_{\text{equiv}} = \frac{1}{\frac{1}{10} + \frac{1}{25} + \frac{1}{15}} = \frac{1}{0.1 + 0.04 + 0.0667} = \boxed{4.84\Omega}$$

Part (b): $I = \frac{V}{R_{\text{equiv}}} = \frac{3\text{ V}}{4.84\Omega} = \boxed{0.62\text{ A}}$

Reveal: Parallel Solution

Self-correct in a different color:

Part (a): $R_{\text{equiv}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$

$$R_{\text{equiv}} = \frac{1}{\frac{1}{10} + \frac{1}{25} + \frac{1}{15}} = \frac{1}{0.1 + 0.04 + 0.0667} = \boxed{4.84\Omega}$$

Part (b): $I = \frac{V}{R_{\text{equiv}}} = \frac{3\text{ V}}{4.84\Omega} = \boxed{0.62\text{ A}}$

Check: $4.84 \ll 10$ (smallest resistor). Current splits: $I_1 = 0.30\text{ A}$, $I_2 = 0.12\text{ A}$, $I_3 = 0.20\text{ A}$!

Learning Objectives

By the end of this section, you will be able to:

- **19.4:** Define electric power and describe the power equation

Learning Objectives

By the end of this section, you will be able to:

- **19.4:** Define electric power and describe the power equation
- **19.4:** Calculate power in circuits

19.4 The Energy Transfer Rate

The Power Law

$$P = IV$$

Power equals current times voltage. Energy per unit time.

19.4 The Energy Transfer Rate

The Power Law

$$P = IV$$

Power equals current times voltage. Energy per unit time.

Units: Watts (W), where $1 \text{ W} = 1 \text{ J/s}$

19.4 The Energy Transfer Rate

The Power Law

$$P = IV$$

Power equals current times voltage. Energy per unit time.

Units: Watts (W), where $1\text{ W} = 1\text{ J/s}$

The Mental Model

A 60-W bulb transfers 60 joules per second from electrical energy to light and heat.

19.4 Three Forms of Power

Using Ohm's law $V = IR$, we can derive alternate forms:

19.4 Three Forms of Power

Using Ohm's law $V = IR$, we can derive alternate forms:

$$P = IV \quad (1)$$

$$P = I^2 R \quad (\text{using } V = IR) \quad (2)$$

$$P = \frac{V^2}{R} \quad (\text{using } I = \frac{V}{R}) \quad (3)$$

19.4 Three Forms of Power

Using Ohm's law $V = IR$, we can derive alternate forms:


$$P = IV \quad (1)$$

$$P = I^2 R \quad (\text{using } V = IR) \quad (2)$$


$$P = \frac{V^2}{R} \quad (\text{using } I = \frac{V}{R}) \quad (3)$$

Choose the form that matches your known quantities.

19.4 The 25-W vs 60-W Mystery

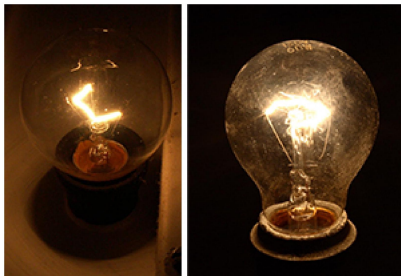


19.4 The 25-W vs 60-W Mystery

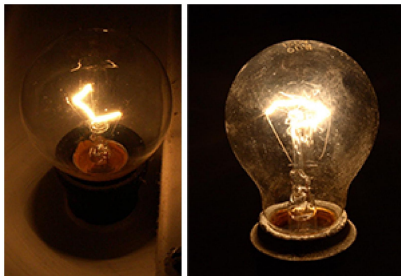

Question: Both run on 120 V. Why different brightness?

19.4 The 25-W vs 60-W Mystery

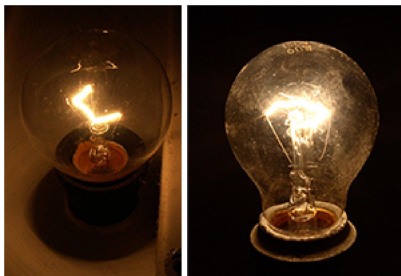

Question: Both run on 120 V. Why different brightness?

The Revelation

They have DIFFERENT resistances! Using $P = \frac{V^2}{R}$, higher power means LOWER resistance.

Attempt: Lightbulb Current

The Challenge (3 min, silent)

A 60-W incandescent bulb operates on 120 V.

Given:

- $P = 60 \text{ W}$
- $V = 120 \text{ V}$

Find: Current through the bulb

Which power formula should you use?

Compare: Power Formula

Turn and talk (2 min):

- 1 Which power formula did you use?
- 2 How did you solve for current?
- 3 What units did you get?

Compare: Power Formula

Turn and talk (2 min):

- 1 Which power formula did you use?
- 2 How did you solve for current?
- 3 What units did you get?

Name wheel: One pair share your approach.

Reveal: Lightbulb Current

Self-correct in a different color:

Start with: $P = IV$

Reveal: Lightbulb Current

Self-correct in a different color:

Start with: $P = IV$

Solve for I: $I = \frac{P}{V}$

Reveal: Lightbulb Current

Self-correct in a different color:

Start with: $P = IV$

Solve for I: $I = \frac{P}{V}$

Substitute: $I = \frac{60 \text{ W}}{120 \text{ V}}$

Reveal: Lightbulb Current

Self-correct in a different color:

Start with: $P = IV$

Solve for I: $I = \frac{P}{V}$

Substitute: $I = \frac{60 \text{ W}}{120 \text{ V}}$

$$I = 0.50 \text{ A}$$

Reveal: Lightbulb Current

Self-correct in a different color:

Start with: $P = IV$

Solve for I: $I = \frac{P}{V}$

Substitute: $I = \frac{60 \text{ W}}{120 \text{ V}}$

$$I = 0.50 \text{ A}$$

Check: Half an ampere - significant current for a light bulb!

What You Now Know

The Revelations

① Current = charge per time: $I = \frac{\Delta Q}{\Delta t}$

What You Now Know

The Revelations

- 1 Current = charge per time: $I = \frac{\Delta Q}{\Delta t}$
- 2 Ohm's law = the pushback equation: $V = IR$

What You Now Know

The Revelations

- 1 Current = charge per time: $I = \frac{\Delta Q}{\Delta t}$
- 2 Ohm's law = the pushback equation: $V = IR$
- 3 Series resistances add: $R_{\text{equiv}} = R_1 + R_2 + \dots$

What You Now Know

The Revelations

- 1 Current = charge per time: $I = \frac{\Delta Q}{\Delta t}$
- 2 Ohm's law = the pushback equation: $V = IR$
- 3 Series resistances add: $R_{\text{equiv}} = R_1 + R_2 + \dots$
- 4 Parallel uses reciprocals: $R_{\text{equiv}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots}$

What You Now Know

The Revelations

- 1 Current = charge per time: $I = \frac{\Delta Q}{\Delta t}$
- 2 Ohm's law = the pushback equation: $V = IR$
- 3 Series resistances add: $R_{\text{equiv}} = R_1 + R_2 + \dots$
- 4 Parallel uses reciprocals: $R_{\text{equiv}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots}$
- 5 Power = energy transfer rate: $P = IV = I^2 R = \frac{V^2}{R}$

Key Equations

$$I = \frac{\Delta Q}{\Delta t} \quad (\text{current}) \quad (4)$$

$$V = IR \quad (\text{Ohm's law}) \quad (5)$$

$$R_{\text{series}} = R_1 + R_2 + \cdots + R_N \quad (6)$$

$$R_{\text{parallel}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_N}} \quad (7)$$

$$P = IV \quad (8)$$

$$P = I^2 R \quad (9)$$

$$P = \frac{V^2}{R} \quad (10)$$

Complete the assigned problems
posted on the LMS