

Concept Items

19.1 Ohm's law 1.

You connect a resistor across a battery. In which direction do the electrons flow?

- The electrons flow from the negative terminal of the battery to the positive terminal of the battery.
- The electrons flow from the positive terminal of the battery to the negative terminal of the battery.

2.

How does current depend on resistance in Ohm's law?

- Current is directly proportional to the resistance.
- Current is inversely proportional to the resistance.
- Current is proportional to the square of the resistance.
- Current is inversely proportional to the square of the resistance.

3.

In the context of electricity, what is resistance?

- Resistance is the property of materials to resist the passage of voltage.
- Resistance is the property of materials to resist the passage of electric current.
- Resistance is the property of materials to increase the passage of voltage.
- Resistance is the property of materials to increase the passage of electric current.

4.

What is the mathematical formula for Ohm's law?

- $V = I^2 R$
- $V = \frac{R}{I}$
- $V = \frac{I}{R}$
- $V = IR$

19.2 Series Circuits 5.


In which circuit are all the resistors connected in series?





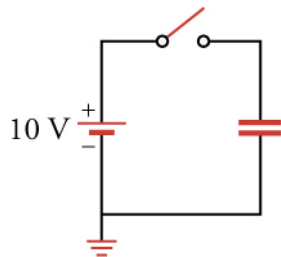6.

What is the voltage and current through the capacitor in the circuit below a long time after the switch is closed?



- a. 0 V, 0 A
- b. 0 V, 10 A
- c. 10 V, 0 A
- d. 10 V, 10 A

19.3 Parallel Circuits 7.

If you remove resistance from a circuit, does the total resistance of the circuit always decrease? Explain.

- a. No, because for a parallel combination of resistors, the resistance through the remaining circuit increases.
- b. Yes, because for a parallel combination of resistors, the resistance through the remaining circuit increases.

8.

Explain why the equivalent resistance of a parallel combination of resistors is always less than the smallest of the parallel resistors.

- a. Adding resistors in parallel gives the current a shorter path through which it can flow, hence decreasing the overall resistance.
- b. Adding resistors in parallel gives the current another path through which it can flow, hence decreasing the overall resistance.
- c. Adding resistors in parallel reduce the number of paths through which the current can flow, hence decreasing the overall resistance.
- d. Adding resistors in parallel gives the current a longer path through which it can flow, hence decreasing the overall resistance.

19.4 Electric Power 9.

To draw the most power from a battery, should you connect a small or a large resistance across its terminals? Explain.

- a. Small resistance, because smaller resistance will lead to the largest power
- b. Large resistance, because smaller resistance will lead to the largest power

10.

If you double the current through a resistor, by what factor does the power dissipated by the resistor change?

- a. Power increases by a factor of two.
- b. Power increases by a factor of four.
- c. Power increases by a factor of eight.
- d. Power increases by a factor of 16.